<<   >>

<<   >>

13   ISBN   9787121038662

10   ISBN   7121038668

            2007-2

        397

                        PDF

            http://www.tushu007.com

<< >>

James W.Nilsson   39

1962   R.G.Brown   Introduction to Linear Systems Analysis   1968   Introduction to Circuits Instruments,and Electronics   1

Chapter 1 Circuit Variables and Circuit Elements 1.1 Circuit Analysis: an Overview 1.2 Voltage, Current, and the Basic Circuit Elements 1.3 The Ideal Basic Circuit Element 1.4 Power and Energy 1.5 Voltage and Current Sources 1.6 Electrical Resistance (OHMÕs Law) 1.7 KirchhoffÕs Laws 1.8 Analysis of a Circuit Containing Dependent SourcesChapter 2 Some Circuit Simplification Techniques 2.1 Source Transformations 2.2 SuperpositionChapter 3 Techniques of Circuit Analysis 3.1 Terminology 3.2 Introduction to the Node-Voltage Method 3.3 The Node-Voltage Method and Dependent Sources 3.4 The Node-Voltage Method: Some Special Cases 3.5 Introduction to the Mesh-Current Method 3.6 The Mesh-Current Method and Dependent Sources 3.7 The Mesh-Current Method: Some Special Cases 3.8 The Node-Voltage Method Versus the Mesh-Current Method 3.9 ThŽvenin and Norton Equivalents 3.10 More on Deriving a ThŽvenin Equivalent 3.11 Maximum Power TransferChapter 4 The Operational Amplifier 4.1 Operational Amplifier Terminals 4.2 Terminal Voltages and Currents 4.3 The Inverting-Amplifier Circuit 4.4 The Summing-Amplifier Circuit 4.5 The Noninverting-Amplifier Circuit 4.6 The Difference-Amplifier Circuit 4.7 The ComparatorChapter 5 The Natural and Step Response of RL and RC Circuits 5.1 The Inductor 5.2 The Capacitor 5.3 Series-Parallel Combinations of Inductance and Capacitance 5.4 Natural Response of RL and RC Circuits 5.5 Step Response of RL and RC Circuits 5.6 The Integrating AmplifierChapter 6 Natural and Step Responses of RLC Circuits 6.1 Introduction to the Natural Response of a Parallel RLC Circuit 6.2 The Forms of the Natural Response of a Parallel RLC Circuit 6.3 The Step Response of a Parallel RLC Circuit 6.4 The Natural and Step Response of a Series RLC CircuitChapter 7 Sinusoidal Steady-State Analysis 7.1 The Sinusoidal Source 7.2 The Sinusoidal Response 7.3 The Phasor 7.4 The Passive Circuit Elements in the Frequency Domain 7.5 KirchhoffÕs Laws in the Frequency Domain 7.6 Circuit Simplifications 7.7 The Node-Voltage Method 7.8 The Mesh-Current Method 7.9 Instantaneous, Average, and Reactive Power 7.10 The rms Value and Power Calculations 7.11 Complex Power and Power CalculationsChapter 8 Balanced Three-Phase Circuits 8.1 Balanced Three-Phase Voltages 8.2 Three-Phase Voltage Sources 8.3 Analysis of the Wye-Wye Circuit 8.4 Analysis of the Wye-Delta Circuit 8.5 Power Calculations in Balanced Three-Phase Circuits 8.6 Measuring Average Power in Three-Phase CircuitsChapter 9 Introduction to Frequency Selective Circuits 9.1 Some Preliminaries 9.2 Low-Pass Filters 9.3 High-Pass Filters 9.4 Bandpass Filters 9.5 Bandreject Filters

<<   >>

PDF

:http://www.tushu007.com